

POTW solution 8/8 - 8/15

We will first solve the following problem algebraically:

We determine how to decompose any binary function of several binary variables as a composition of \hat{A} AND, \hat{V} OR and \hat{N} NOT gates/operations.

For example:

A	B	f
0	0	0
0	1	1
1	0	0
1	1	1

We can decompose f as $(\hat{N}A \hat{A} B) \hat{V} (A \hat{A} B)$

Our main strategy is to use the 'linearity' of \hat{V} operation.

By which we mean thinking of \hat{V} as $+$ we have $T + F = T$; $T + T = T$

$T + F + F = T$ and so on.

The central idea is to write any function 'f' as a sum of 'bump' functions, analogous to a basis.

A 'bump' function is any function g which is 1 on (T) for one particular tuple of the variables and zero for all others.

For example:

A	B	g
0	0	0
0	1	1
1	0	0
1	1	0

g is the bump corresponding to $(A, B) = (0, 1)$

Notice that any bump function can be written as the 'product' of the variables, for eg. $g = (\neg A) \wedge (B)$ for our previous example.

It is clear that any variable X with a value of 0 in the bump tuple occurs with a ' \neg ' in front of it in the product.

It can be seen now that any general function can be written as the 'sum' of 'bump' functions for the tuples on which it assumes the value 1

for eg.

A	B	C	f	
0	0	0	1	$g_1 = (\neg A) \wedge (\neg B) \wedge (\neg C)$
0	0	1	0	
0	1	0	0	
0	1	1	1	$g_2 = (\neg A) \wedge B \wedge C$
1	0	0	0	
1	0	1	1	$g_3 = A \wedge (\neg B) \wedge C$
1	1	0	0	
1	1	1	1	$g_4 = A \wedge B \wedge C$

clearly $f = g_1 \vee g_2 \vee g_3 \vee g_4$

Notice that this is certainly not the most efficient way of decomposing f , but it gets the job done.

Now all that needs to be done is to express \vee , \wedge and \neg as a composition of NANDs.

But this is clear:

$$\neg A = A \otimes A$$

$$A \wedge B = (A \otimes B) \otimes (A \otimes B) = \neg(A \otimes B)$$

$$A \vee B = (\neg A) \otimes (\neg B)$$

Finally building a NAND gate from transistors is clear from the following circuit:

